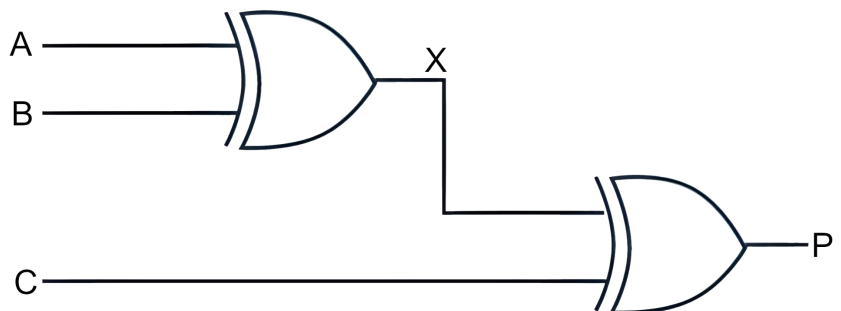



3 bit Even Parity Generator.

A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



Assume we have a 3-bit even parity generator. Suppose the three inputs A, B and C are applied to the circuit and the output bit is the parity bit P. The total number of 1's must be even to generate the even parity bit P. Based on the above circuit, we see that we need 2 gates XOR where $X = A \text{ xor } B$ and $P = X \text{ xor } C$. X acts as the output of the first XOR and input of the second. In all 3 circuits the result of the simulation is as follows

Run Time: 80ns

 

> For instance:

At 0 ns $A = 0, B = 0, C = 0 \rightarrow P = 0$

At 10 ns έχουμε $A = 0, B = 0, C = 1 \rightarrow P = 1$

At 40 ns έχουμε $A = 1, B = 0, C = 0 \rightarrow P = 1$

At 60 ns έχουμε $A = 1, B = 1, C = 0 \rightarrow P = 0$

By comparing the simulation results with the truth table we see that we have achieved the desired result

Circuit Implementations:

*The testbench remains the same for all three models.

> DataFlow Model:

```
library IEEE;
use IEEE.std_logic_1164.all;

entity ParityGenerator is
    port(A,B,C: in bit; X: inout bit; P: out bit);
end ParityGenerator;

architecture dataflow of ParityGenerator is
begin
    X <= A xor B;
    P <= X xor C;
end dataflow;
```

> Behavioural/Algorithmic Model:

```
library IEEE;
use IEEE.std_logic_1164.all;
entity ParityGenerator is
    port(A,B,C: in bit; X: inout bit; P: out bit);
end ParityGenerator;

architecture algorithmic of ParityGenerator is
begin
    -- Process for assigning value to X
    p0: process (A,B)
        variable s: bit_vector (1 downto 0);
    begin
        s := A & B;
        if s = "00" then X <= '0';
        elsif s = "01" then X <= '1';
        elsif s = "10" then X <= '1';
        elsif s = "11" then X <= '0';
        end if;
    end process;

    -- Process for assigning value to P
    p1: process (X,C)
        variable s: bit_vector (1 downto 0);
    begin
        s := X & C;
        if s = "00" then P <= '0';
        elsif s = "01" then P <= '1';
        elsif s = "10" then P <= '1';
        elsif s = "11" then P <= '0';
        end if;
    end process;
end algorithmic;
```

> Structural Model:

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity ParityGenerator is  
    port(A,B,C: in bit; X: inout bit; P: out bit);  
end ParityGenerator;
```

```
entity xor2 is -- XOR 2 εισόδων  
    port (X1,X2: in bit; O: out bit);  
end xor2;
```

architecture structure of ParityGenerator is

```
    component xor2  
        port(X1,X2: in bit; O: out bit);  
    end component;
```

```
begin  
    u0: xor2 port map (A,B,X);  
    u1: xor2 port map (X,C,P);  
end structure;
```

architecture behave of xor2 is

```
begin  
    O<= X1 xor X2;  
end behave;
```

Testbench:

```
library IEEE;  
use IEEE.std_logic_1164.all;
```

```
entity test_ParityGenerator is  
end test_ParityGenerator;
```

architecture testbench of test_ParityGenerator is

```
    component ParityGenerator  
        port(A,B,C: in bit; X: inout bit; P: out bit);  
    end component;  
    signal tb_A: bit;  
    signal tb_B: bit;  
    signal tb_C: bit;  
    signal tb_P: bit;
```

```
begin  
    u0: ParityGenerator port map(  
        A => tb_A,  
        B => tb_B,  
        C => tb_C,  
        P => tb_P);
```

```
process
begin
tb_C <= '0' ;
tb_B <= '0' ;
tb_A <= '0' ;
wait for 10 ns;

tb_C <= '1' ;
tb_B <= '0' ;
tb_A <= '0' ;
wait for 10 ns;

tb_C <= '0' ;
tb_B <= '1' ;
tb_A <= '0' ;
wait for 10 ns;

tb_C <= '1' ;
tb_B <= '1' ;
tb_A <= '0' ;
wait for 10 ns;

tb_C <= '0' ;
tb_B <= '0' ;
tb_A <= '1' ;
wait for 10 ns;

tb_C <= '1' ;
tb_B <= '0' ;
tb_A <= '1' ;
wait for 10 ns;

tb_C <= '0' ;
tb_B <= '1' ;
tb_A <= '1' ;
wait for 10 ns;

tb_C <= '1' ;
tb_B <= '1' ;
tb_A <= '1' ;
wait for 10 ns;

end process;
end testbench;
```