
 


## 4 bit Counter

### Asynchronous 4 bit Counter

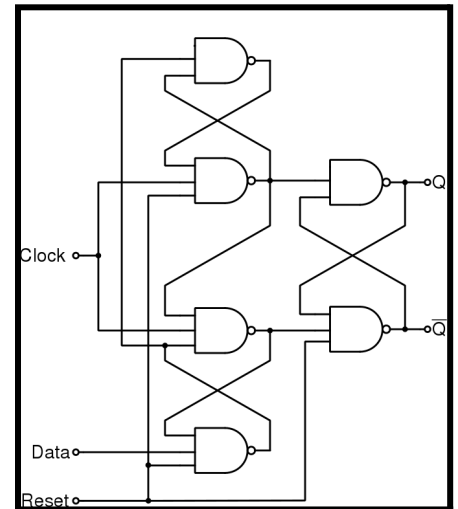


### D flip-flop




Implementing a 4-bit asynchronous counter requires the interconnection of four D Flip-Flops. The clock input is connected to the first Flip-Flop. The remaining Flip-Flops receive their clock signal input from the Q' output of the previous Flip-Flop. In the counter the Flip-Flops are connected in toggle mode, so when the clock input is connected to the first flip flop D-FF0, then its output after one clock pulse will become 20ns. The q outputs of each D-FF represent the metre reading.

The simulation results are as follows
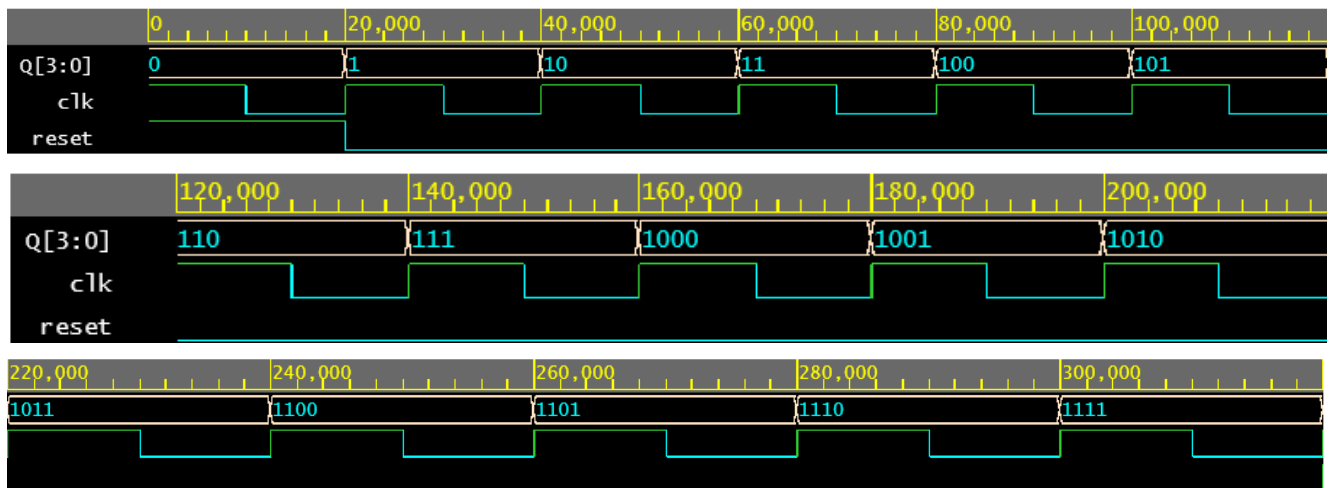
#### Count from 0 to 15 - Run Time: 320ns


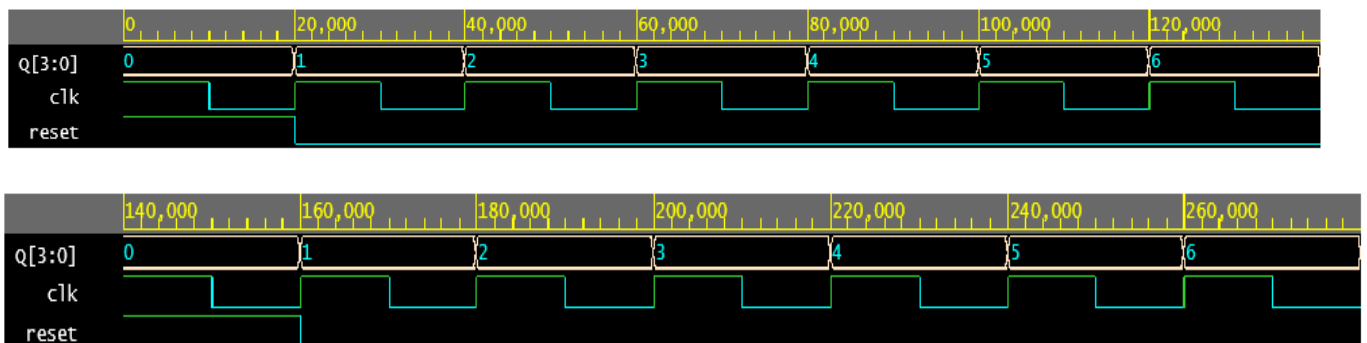
#### Count from 0 to 6 with repetition - Run Time: 270ns



### **Behavioural/Algorithmic model:**

```
library IEEE;
use IEEE.std_logic_1164.all;
-- Creating a Positively Triggered D Flip - Flop
entity D_FlipFlop is
    port ( FFclk,FFreset,FFD: in bit; FFq: out bit);
end D_FlipFlop;
```

architecture Algorithmic of D\_FlipFlop is

```
begin
    process(FFd,FFclk, FFreset)
    begin
        -- Create a rollback feature
        if (FFreset = '1') then
            FFq <= '0';
        -- Value change event
        elsif (FFclk = '1') and FFclk'event then
            FFq <= FFd;
        end if;
    end process;
end Algorithmic;
```

-- Creating a 4-bit counter

```
entity counter_4bit is
    Port ( clk,reset : in  bit;
          Q: out  bit_vector(3 downto 0));
end counter_4bit;
```

architecture Algorithmic of counter\_4bit is

```
    component D_FlipFlop
        port ( FFclk,FFreset,FFD: in bit; FFq: out bit);
    end component;
```

signal q0, q1, q2,q3: bit;

begin

-- Creation of the 4 Flip-Flops and the corresponding bit assignment between them.  
-- eg FF0 output FFq to be assigned to q0 and then q0 to be mapped as FF1's clk input  
-- The output FFq of FF1 is assigned to q1 and then q1 is assigned as the clk input of FF2. ....  
-- etc.

```
FF0: D_FlipFlop
port map(FFclk => clk, FFreset => reset, FFd => (not q0), FFq => q0);
FF1: D_FlipFlop
port map(FFclk =>(not q0), FFreset => reset, FFd => (not q1), FFq => q1);
FF2: D_FlipFlop
port map(FFclk => (not q1), FFreset => reset, FFd => (not q2), FFq => q2);
FF3: D_FlipFlop
port map(FFclk => (not q2),FFreset => reset, FFd => (not q3),FFq => q3);
-- Output
    Q <= q3 & q2 & q1 & q0;
end Algorithmic;
```

## Testbench

Testbench

library IEEE;

use IEEE.std\_logic\_1164.all;

entity test\_counter\_4bit is

end test\_counter\_4bit;

architecture testbench of test\_counter\_4bit is

component counter\_4bit

port(

clk,reset : in bit;

Q: out bit\_vector(3 downto 0));

end component;

signal clk:bit;

signal reset:bit;

signal Q:bit\_vector(3 downto 0);

begin

test: counter\_4bit port map (

clk=>clk,

reset=>reset,

Q=>Q);

process

begin

-- This particular testbench counts up to 6

-- Reset assignment. Depending on the number you wish to count

-- need to add appropriate number clk<='1'? reset<='0'; and clk<='0'; reset <='0';

clk<='1'; reset<='1';

wait for 10 ns;

clk<='0'; reset<='1';

wait for 10 ns;

--1

clk<='1'; reset<='0';

wait for 10 ns;

clk<='0'; reset <='0';

wait for 10 ns;

--2

clk<='1'; reset<='0';

wait for 10 ns;

clk<='0'; reset<='0';

wait for 10 ns;

--3

clk<='1'; reset<='0';

wait for 10 ns;

clk<='0'; reset<='0';

wait for 10 ns;

--4

```
clk<='1'; reset<='0';  
wait for 10 ns;  
clk<='0'; reset<='0';  
wait for 10 ns;
```

--5

```
clk<='1'; reset<='0';  
wait for 10 ns;  
clk<='0'; reset<='0';  
wait for 10 ns;
```

--6

```
clk<='1'; reset<='0';  
wait for 10 ns;  
clk<='0'; reset<='0';  
wait for 10 ns;
```

```
end process;  
end testbench ;
```